

HALF ADDER

EXP.NO: 27

AIM:

To design and implement the two bit half adder using Logisim simulator.

PROCEDURE:

- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the XOR gate and AND gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.

TRUTH TABLE:

A	B	S	C
0	0	0	0
0	1	1	0

1	0	1	0
1	1	0	1

$S = A \text{ XOR } B$ $C = A \text{ AND } B$

OUTPUT



